



‘समानो मन्त्रः समितिः समानी’

UNIVERSITY OF NORTH BENGAL

B.Sc. Honours 1st Semester Examination, 2021

CC2-COMPUTER SCIENCE (13)

COMPUTER SYSTEM ARCHITECTURE

Time Allotted: 2 Hours

Full Marks: 40

*The figures in the margin indicate full marks.
All symbols are of usual significance.*

1. Answer any **five** questions: 1×5 = 5
 - (a) Write the name of basic logic gates.
 - (b) Define Boolean algebra.
 - (c) Which one is faster between the RISC and CISC architecture?
 - (d) Convert the given binary number $(10100110)_2$ to decimal number.
 - (e) Write the full forms of VLSI and CMOS.
 - (f) Define the term micro-operation.
 - (g) What is a flip-flop?
 - (h) How many minterm are there in an n variable truth table?

2. Answer any **three** questions: 5×3 = 15
 - (a) Compare the Combinational circuits and Sequential circuits.
 - (b) Convert the given number with the indicated base $(4012)_5$ to decimal and binary.
 - (c) Discuss the arrangements of Three-variable and Four-variable K-map.
 - (d) Write a note on SR flip-flop.
 - (e) Write a note on Hit ratio.

3. Answer any **two** questions: 10×2 = 20
 - (a) What is multiplexer? With appropriate diagram explain in detail a 4-to-1-line multiplexer.
 - (b) Discuss the SOP form of Boolean expression. Reduce the following Boolean expression in SOP form using K-map.
$$F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 5, 10, 11, 15)$$
 - (c) Explain Half-Adder and Full-Adder with suitable Truth tables and Logic diagrams.
 - (d) Discuss Cache memory and explain the Associative mapping with suitable example.

—x—